

Lab Experiment # 07

The Story of Minterms and Maxterms

Objectives

Learn how implement logic functions using the standard forms: Sum of Products and Product of Sums.

Background

We can write expressions in many ways, but some ways are more useful than others


A sum of products (SOP) expression contains: Only OR (sum) operations at the “outermost” level and each term that is summed must be a product of literals

The advantage is that any sum of products expression can be implemented using a three-level circuit

- literals and their complements at the first level
- AND gates at the second level
- a single OR gate at the third level

Example:

$$f(x,y,z) = y' + x'yz' + xz$$

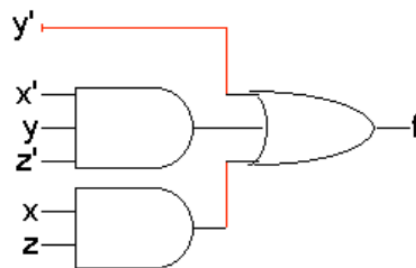

Notice that the NOT gates are implicit and that literals are reused.

A minterm is a special product of literals, in which each input variable appears exactly once.

A function with n variables has 2^n minterms (since each variable can appear complemented or not)

Example:

A three-variable function, such as $f(x,y,z)$, has $2^3 = 8$ minterms:

Each minterm is true for exactly one combination of inputs:

Those minterms are: $x'y'z'$ $x'y'z$ $x'yz'$ $x'yz$ $xy'z'$ $xy'z$ xyz' xyz

A Minterm is true when:

Minterm	When the minterm is True			Minterm ID
$x'y'z'$	$x=0,$	$y=0,$	$z=0$	m0
$x'y'z$	$x=0,$	$y=0,$	$z=1$	m1
$x'yz'$	$x=0,$	$y=1,$	$z=0$	m2
$x'yz$	$x=0,$	$y=1,$	$z=1$	m3
$xy'z'$	$x=1,$	$y=0,$	$z=0$	m4
$xy'z$	$x=1,$	$y=0,$	$z=1$	m5
xyz'	$x=1,$	$y=1,$	$z=0$	m6
xyz	$x=1,$	$y=1,$	$z=1$	m7

Sum of Minterms (or Sum of Products)

Every function can be written as a sum of minterms, which is a special kind of sum of products form

The sum of minterms form for any function is unique

If you have a truth table for a function, you can write a sum of minterms expression just by picking out the rows of the table where the function output is 1.

Example

$$\begin{aligned}
 f &= x'y'z' + x'y'z + x'yz' + x'yz + xyz' \\
 &= m_0 + m_1 + m_2 + m_3 + m_6 \\
 &= \Sigma m(0,1,2,3,6)
 \end{aligned}$$

The dual idea: products of sums

A product of sums (POS) expression contains: Only AND (product) operations at the “outermost” level, Each term must be a sum of literals.


Product of sums expressions can be implemented with three-level circuits

- literals and their complements at the first level
- OR gates at the first level
- a single AND gate at the second level

• Compare this with sums of products

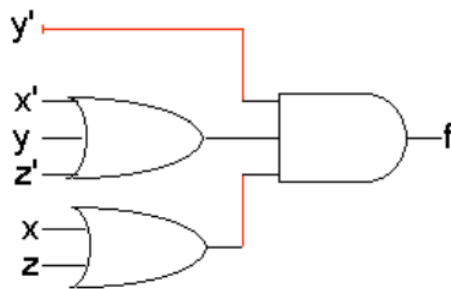Example

$$f(x, y, z) = y' \cdot (x' + y + z') \cdot (x + z)$$



A maxterm is a sum of literals, in which each input variable appears exactly once.

A function with n variables has 2ⁿ maxterms

Example

A three-variable function f(x,y,z) has 8 maxterms

Each maxterm is false for exactly one combination of inputs:

Those maxterms are: x'+y'+z' x'+y'+z x'+y+z' x'+y+z x+y'+z' x+y'+z x+y+z' x+y+z

Maxterm Is false when:

Maxterm	When the maxterm is false	Maxterm ID
$x + y + z$	$x=0, y=0, z=0$	M0
$x + y + z'$	$x=0, y=0, z=1$	M1
$x + y' + z$	$x=0, y=1, z=0$	M2
$x + y' + z'$	$x=0, y=1, z=1$	M3
$x' + y + z$	$x=1, y=0, z=0$	M4
$x' + y + z'$	$x=1, y=0, z=1$	M5
$x' + y' + z$	$x=1, y=1, z=0$	M6
$x' + y' + z'$	$x=1, y=1, z=1$	M7

Every function can be written as a unique product of maxterms

If you have a truth table for a function, you can write a product of maxterms expression by picking out the

rows of the table where the function output is 0. (Be careful if you're writing the actual literals!)

$$f = (x' + y + z).(x' + y + z').(x' + y' + z')$$

$$= M4.M5.M7 = \Pi M(4,5,7)$$

$$f' = (x + y + z).(x + y + z').(x + y' + z).(x + y' + z').(x' + y' + z)$$

$$= M0.M1.M2.M3.M6 = \Pi M(0,1,2,3,6)$$

Minterms and maxterms are related

Any minterm m_i is the complement of the corresponding maxterm M_i

For example, $m4' = M4$ because $(xy'z')' = x' + y + z$

Minterm	Shorthand	Maxterm	Shorthand
$x'y'z'$	m0	$x + y + z$	M0
$x'y'z$	m1	$x + y + z'$	M1
$x'yz'$	m2	$x + y' + z$	M2
$x'yz$	m3	$x + y' + z'$	M3
$xy'z'$	m4	$x' + y + z$	M4
$xy'z$	m5	$x' + y + z'$	M5
xyz'	m6	$x' + y' + z$	M6
xyz	m7	$x' + y' + z'$	M7

Converting between standard forms

We can convert a sum of minterms to a product of maxterms

- In general, just replace the minterms with maxterms, using maxterm numbers that don't appear in the sum of minterms:
- The same thing works for converting from a product of maxterms to a sum of minterms

Example

From before

$$f = \Sigma m(0,1,2,3,6)$$

$$\text{and } f' = \Sigma m(4,5,7)$$

$$= m4 + m5 + m7$$

$$\text{complementing } (f')' = (m4 + m5 + m7)'$$

$$\text{so } f = m4' . m5' . m7' \quad [\text{DeMorgan's law}]$$

$$= M4 . M5 . M7$$

$$= \Pi M(4,5,7)$$

Lab Tasks

Task 1: Three-input Boolean functions

Given the following truth table of a three-input logic circuit


A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Write the above function in the two standard forms


$$F(A, B, C) = \Sigma (\quad)$$

$$F(A, B, C) = \Pi(\quad)$$

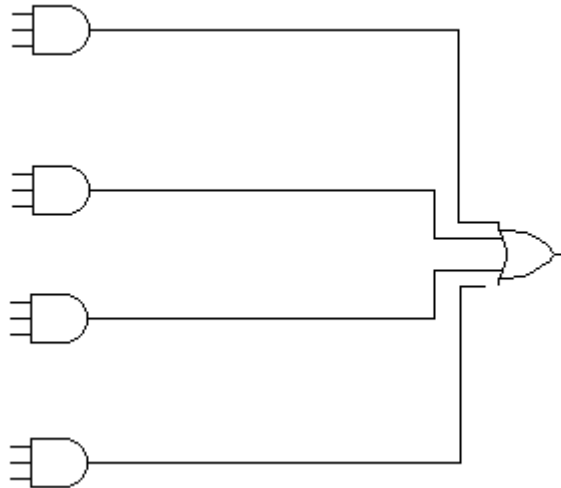Draw a circuit that implements the above logic function (use minterms only)



Draw a circuit that implements the above logic function (use maxterms only)

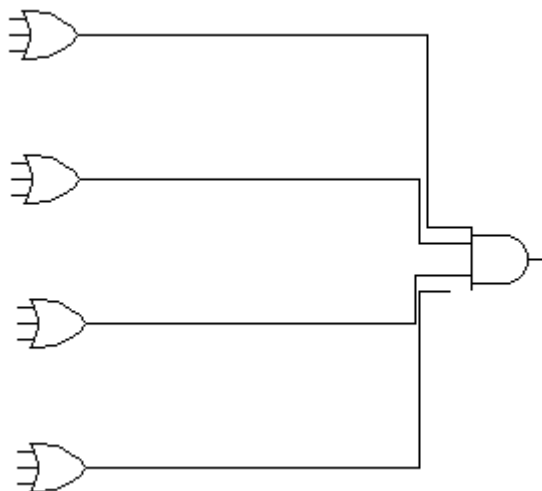

Task 2: Three-input Boolean functions

Simplify (using k-maps) the function presented in Task 1 of this lab. Draw the simplified form of the function on EWB. Use the Logic Converter of EWB to generate the truth table of the simplified circuit.


A	B	C	F (simplified)
0	0	0	
0	0	1	

0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Task 3: Four-input Boolean functions

Draw the following logic function using EWB

$$F(A, B, C, D) = \Sigma(6, 8, 9, 10, 11, 12, 13, 14)$$

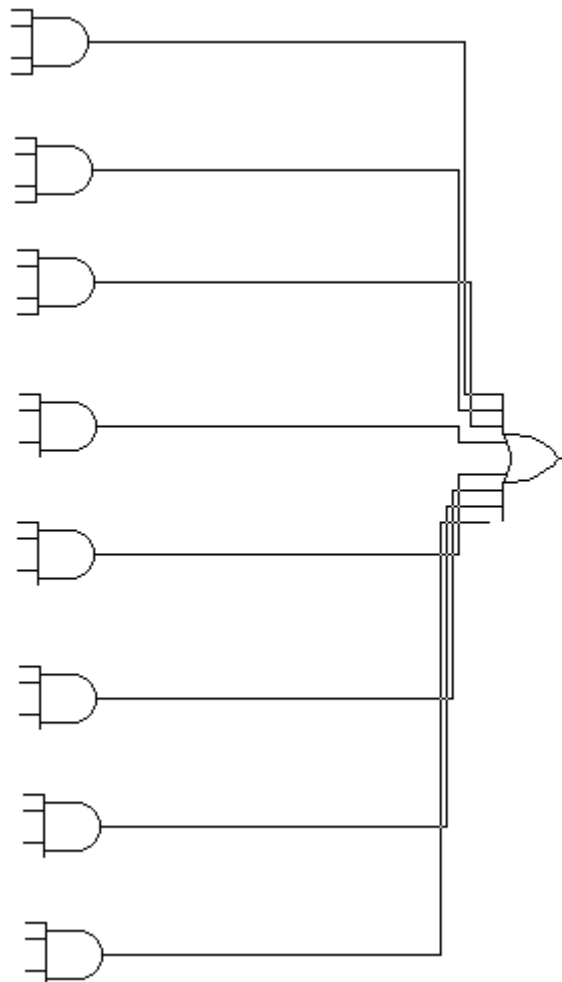

Task 4: Four-input Boolean functions

Simplify (using k-maps) the function presented in Task 3 of this lab. Draw the simplified form of the function on EWB. Use the Logic Converter of EWB to generate the truth table of the simplified circuit.

	A	B	C	D	F
0	0	0	0	0	

1	0	0	0	1	
2	0	0	1	0	
3	0	0	1	1	
4	0	1	0	0	
5	0	1	0	1	
6	0	1	1	0	
7	0	1	1	1	
8	1	0	0	0	
9	1	0	0	1	
10	1	0	1	0	
11	1	0	1	1	
12	1	1	0	0	
13	1	1	0	1	
14	1	1	1	0	
15	1	1	1	1	

Task 5: Simplifying 4-variable functions

Simplify and implement (using EWB) the following function

$$F(a, b, c, d) = (a'+b'+d')(a+b'+c')(a'+b+d')(b+c'+d')$$

Draw you circuit below

Task 6: Simplifying 4-variable functions: SOP

Draw a NAND logic diagram that implements the complement of the following function

$$F(A, B, C, D) = \Sigma(0, 1, 2, 3, 4, 8, 9, 12)$$

Draw you circuit below

Task 7: Simplifying 4-variable functions: POS

Draw a logic diagram that implements the following function

$$F(A, B, C, D) = \Pi(0, 1, 2, 3, 4, 8, 9, 12)$$

Draw you circuit below