

Lab Experiment # 09


Building logic circuits using Multiplexers

Objectives

- To learn how to build combinational logic circuits using multiplexers.

Background

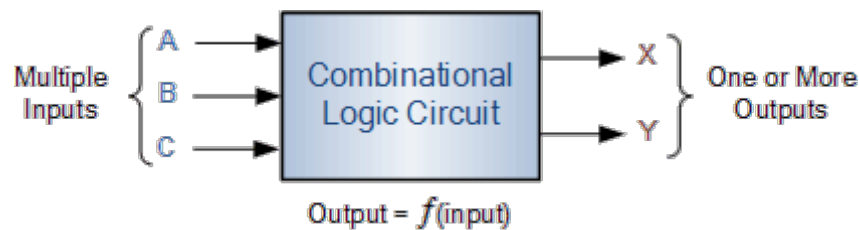
In a **Combinational Logic Circuit**, the output is dependant at all times on the combination of its inputs. Some examples of a combinational circuit include **Multiplexers**, **De-multiplexers**, **Encoders**, **Decoders**, **Full and Half Adders** etc.



A **Multiplexer** is a combination of logic gates resulting into circuits with two or more inputs (data inputs) and one output.

4 Channel Multiplexer using Logic Gates

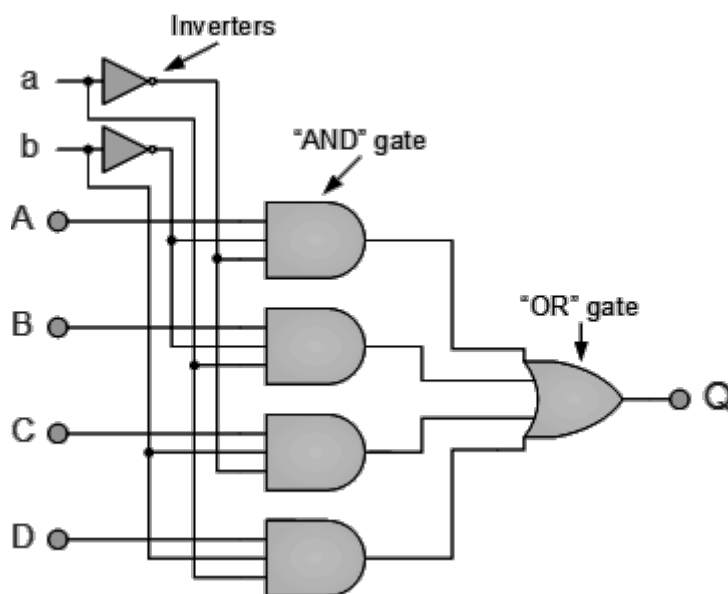The following circuit shows a 4x1 mux. Based on the binary value placed at the inputs "a" and "b", what will appear at the circuit output Q is one of the following values: A, B, C, or D.




The circuit above is implemented based on the following truth table.


a	b	Q
0	0	A
0	1	B
1	0	C
1	1	D

Drawing Multiplexers in EWB:

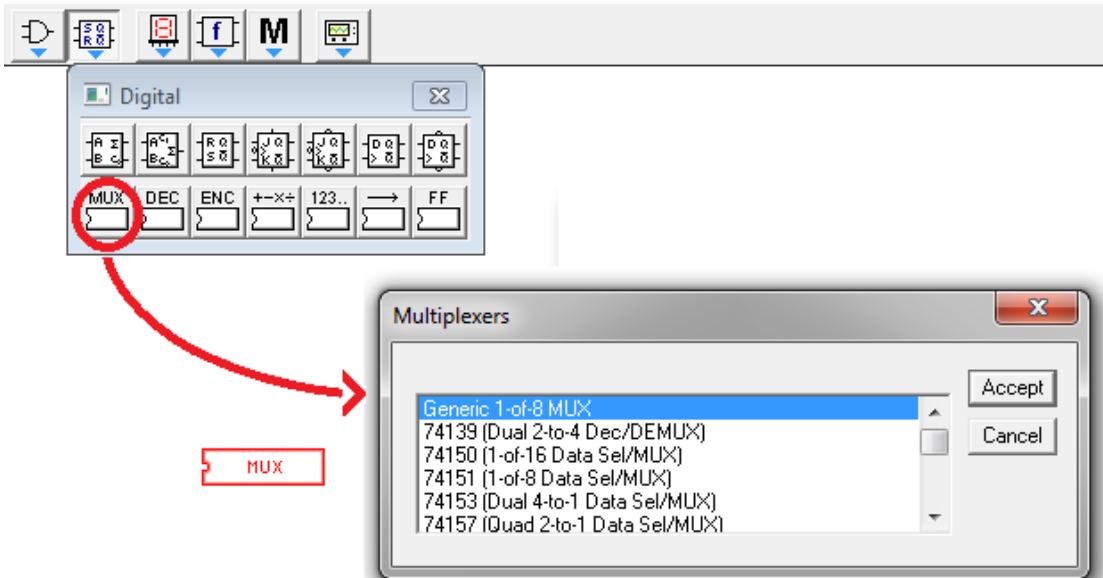
Task: Draw the previous lab examples using EWB, follow the steps below to implement Multiplexers and Decoders.



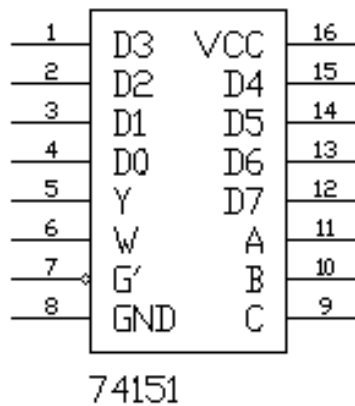Then choose 74151 (1-of-8 Data Sel/MUX) from the list:



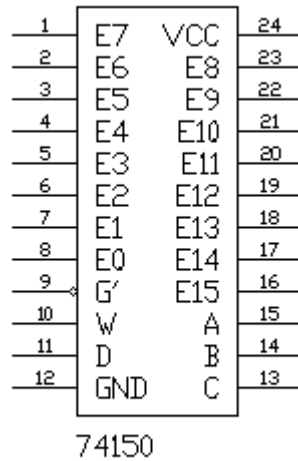You may also choose 74150 (1-of-16 Data Sel/Mux) as follows



NOTE: the “A” line in the multiplexer is the least significant bit, while “C” is the most significant bit.

Data selector/multiplexer truth table:

Select			Strobe	Outputs	
C	B	A	G'	W	Y
x	x	x	1	1	0
0	0	0	0	D0'	D0
0	0	1	0	D1'	D1
0	1	0	0	D2'	D2
0	1	1	0	D3'	D3
1	0	0	0	D4'	D4
1	0	1	0	D5'	D5
1	1	0	0	D6'	D6
1	1	1	0	D7'	D7

Multiplexers can be used to synthesize logic functions


4-to-1 MUX can realize any 3-variable function, 8-to-1 MUX can realize a 3-variable or 4-variable function, in general 2^n -to-1 MUX can realize an $(n + 1)$ -variable and n -variable function.

Example: realizing functions using Multiplexers

The function

$$F = A'BC + AB' + AC'$$

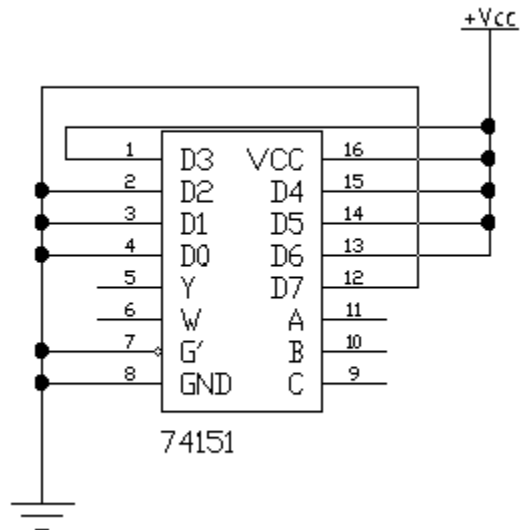Can be implemented using an 8-1 mux as follows




Example: realizing functions using Multiplexers

The function

$$F = A'C' + B'C' + C'D + ABCD'$$

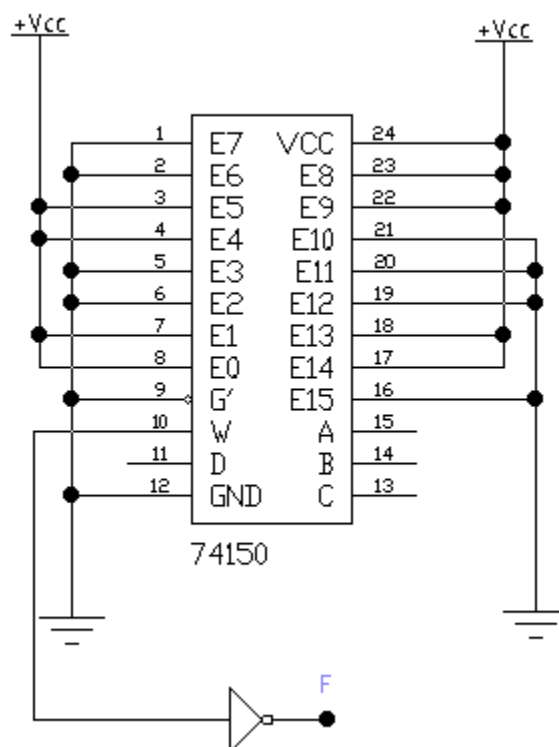Can be implemented using an 8-1 mux as follows



Example: realizing a 4-variable function using 8-to-1 Multiplexer


$$F(A, B, C, D) = A'B'C'D' + A'B'C'D + A'B'CD + A'BC'D' + AB'C'D' + ABC'D' + ABC'D + ABCD$$

Truth table:

	A	B	C	D	F	
0	0	0	0	0	1	F=1
1	0	0	0	1	1	

2	0	0	1	0	0	F=D
3	0	0	1	1	1	
4	0	1	0	0	1	F=D'
5	0	1	0	1	0	
6	0	1	1	0	0	F=0
7	0	1	1	1	0	
8	1	0	0	0	1	F=D'
9	1	0	0	1	0	
10	1	0	1	0	0	F=0
11	1	0	1	1	0	
12	1	1	0	0	1	F=1
13	1	1	0	1	1	
14	1	1	1	0	0	F=D
15	1	1	1	1	1	

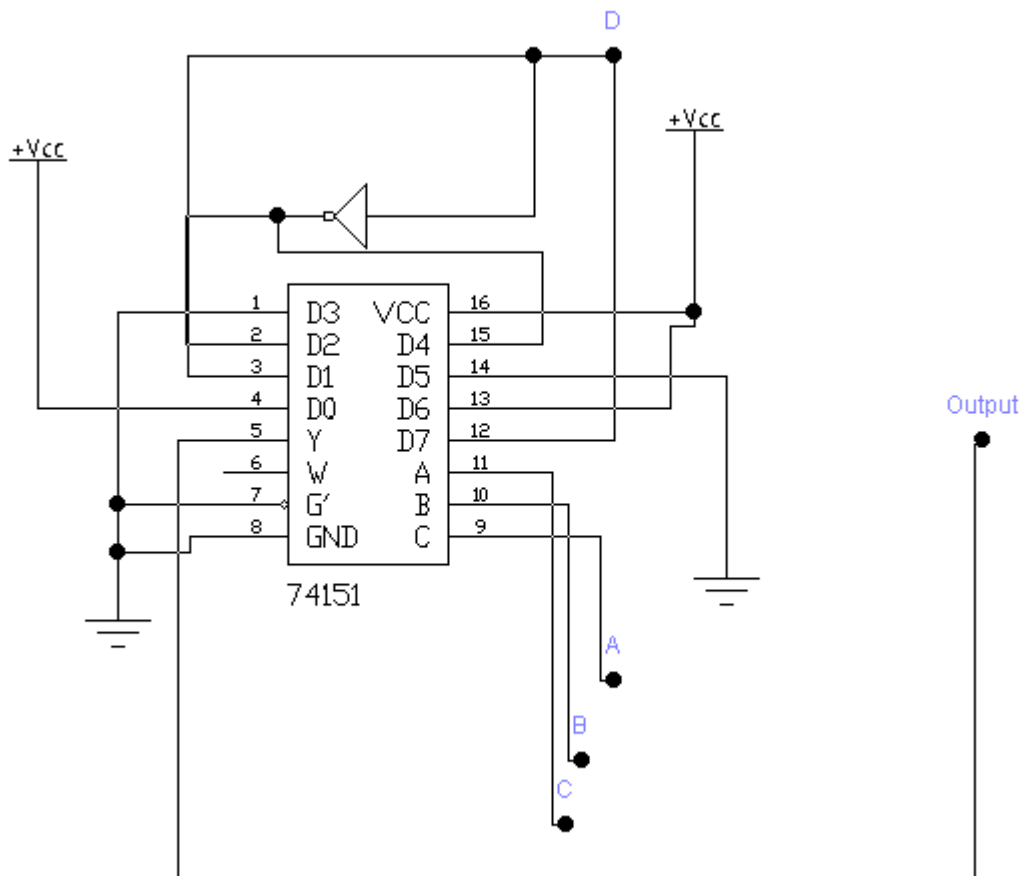To implement this function using EWB, you draw the following circuit:



Lab Tasks

Task 1: Implementing single-output circuits using muxes

Implement the following function using one 8x1 multiplexer


$$F(A, B, C, D) = A'B'C'D' + A'B'C'D + A'B'CD + A'BC'D' + AB'C'D' + ABC'D + ABCD$$

Note: this example has already been solved above. Just draw the circuit using EWB.

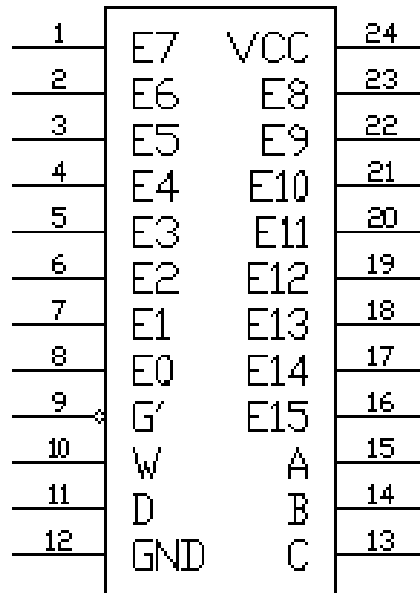Task 2: Implementing single-output circuits using muxes

Implement the following function using one 16x1 multiplexer

$$F(A, B, C, D) = A'C'B + AB'C' + B'C'D + ABCD'$$




74150

Task 3: Implementing single-output circuits using muxes

Implement the following function using one 8x1 multiplexer

$$F(A, B, C, D) = A'C'B + AB'C' + B'C'D + ABCD'$$

	A	B	C	D	F
0	0	0	0	0	
1	0	0	0	1	
2	0	0	1	0	
3	0	0	1	1	
4	0	1	0	0	
5	0	1	0	1	
6	0	1	1	0	
7	0	1	1	1	
8	1	0	0	0	
9	1	0	0	1	
10	1	0	1	0	
11	1	0	1	1	
12	1	1	0	0	
13	1	1	0	1	
14	1	1	1	0	
15	1	1	1	1	

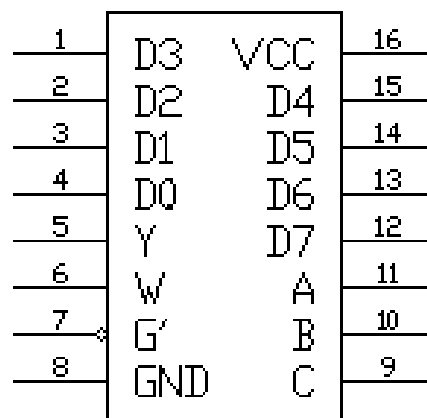


74151


Task 4: Problems with verbal description

Design a combinational circuit (using two 8-to-1 multiplexers) with three inputs, and one output to implement the following function.

	A	B	C	D	F
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	1

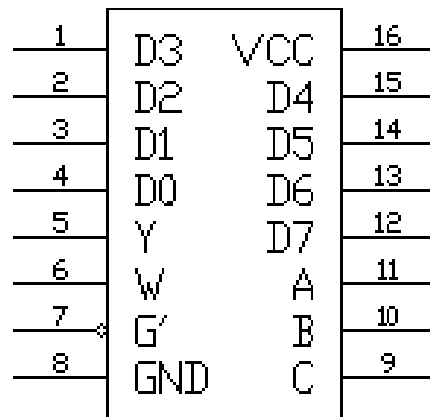

74151

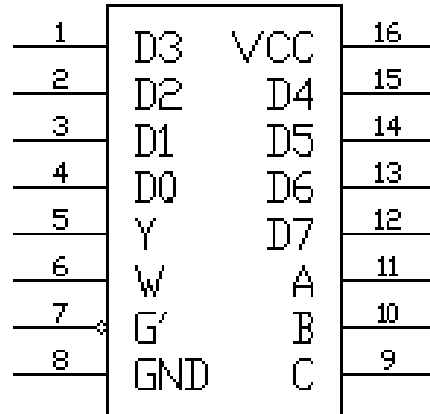

74151